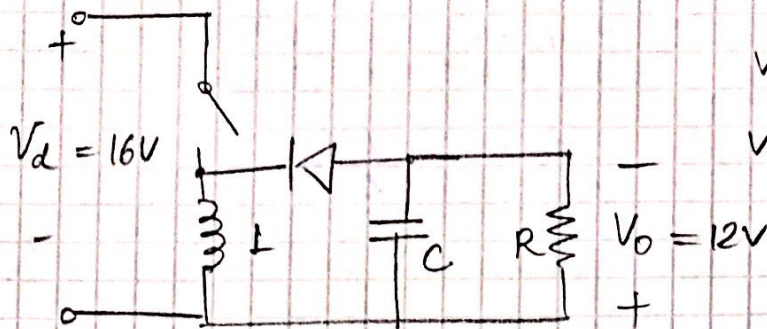


# EE464 HW1

Q1 | Buck-boost converter.



$$\checkmark f_s = 50 \text{ kHz}$$


$$\checkmark 24 \text{ W}$$

$$\checkmark \frac{\Delta V_o}{V_o} \leq 0.02$$

$$\frac{12}{16} = \frac{D}{1-D}$$

$$D = \frac{3}{7}$$

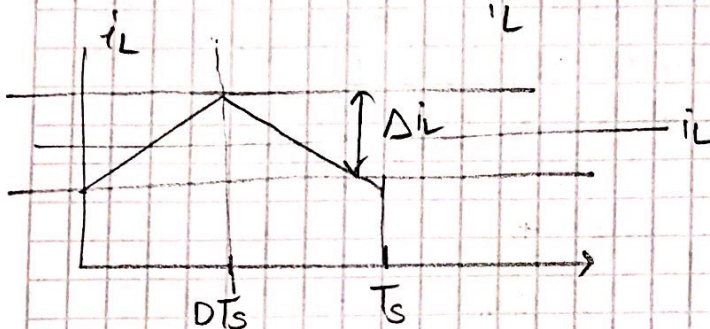a)  $\perp$  so that  $\frac{\Delta i_L}{i_L} = 0.1$  ?



$$V_L = L \frac{di_L}{dt}$$

since the waveform is linear,

$$\frac{V_L}{L} = \frac{\Delta i_L}{\Delta t} \rightarrow \Delta i_L = \frac{V_L \Delta t}{L}$$

$$\Delta i_L = \frac{16 \text{ V} \cdot 3}{7 \cdot 50 \text{ kHz} \cdot L}$$

Since we know the converter is rated 24 W, assuming a lossless operation,

$$P_{out} = V_{out} i_{in} = 24 \text{ W} \rightarrow i_{in} \cdot 16 = 24 \text{ W}$$

$$i_{in} = \frac{3}{2} \text{ A}$$


$$\text{Given } \frac{\Delta i_L}{i_L} = 0.1 \rightarrow \frac{\frac{48}{350 \text{ k} \cdot L}}{\frac{3}{2}} = \frac{1}{10}$$

$$\rightarrow \frac{32}{350 \text{ k} \cdot L} = \frac{1}{10} \rightarrow L \approx 0.914 \text{ mH}$$



b)  $C$  so that  $\frac{\Delta V_{out}}{V_{out}} = 0,02$  ?

Consider the ON cycle:

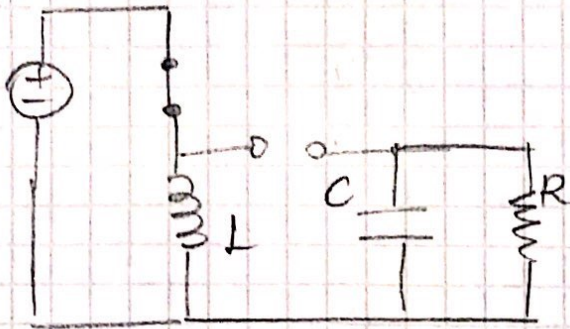

$$i_o = \frac{24W}{12V} = 2A$$

The capacitor will supply the output.  
Assuming a constant current at the output

$$i_o = C \frac{\Delta V_o}{\Delta t}$$

$$2A = C \cdot \frac{\Delta V_o}{(DT_s)}$$


$$\frac{\Delta V_o}{V_o} = 0,02$$

$$\rightarrow \Delta V_o = 0,24$$

$$C = \frac{2 \cdot 3}{7,50k \cdot 0,24} \approx \boxed{71,43 \mu F}$$

c) Choose commercial products.


ON

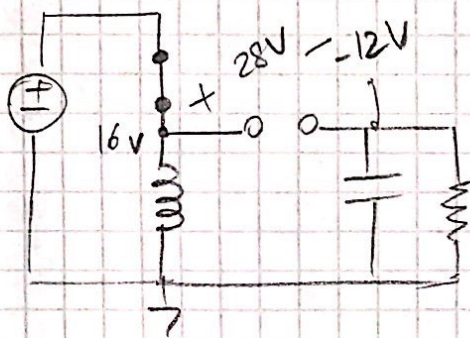

→ D should be able to withstand  $-28V$ .

→ The switch needs to allow an average current of  $\frac{4}{3}A$ .

OFF

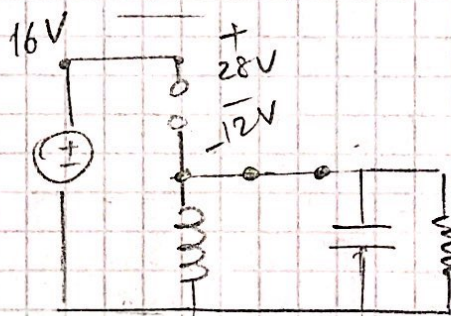

→ D should be able to carry 2A current.

→ The switch needs to be able to withstand 28V.

- L → watch out for the current rating:  $1,5A + 0,1\% \approx 1,65A_{peak}$
- C → watch out for the voltage rating:  $12V + 0,02\% = 12,24V_{peak}$