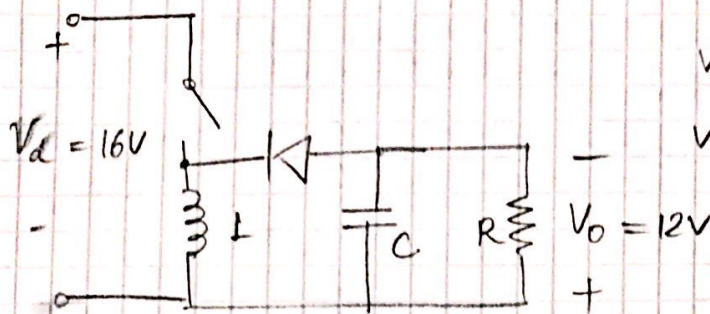


EE464 HW1

Q1 | Buck-boost converter.




$$f_s = 50 \text{ kHz}$$

$$P = 24 \text{ W}$$

$$\frac{\Delta V_o}{V_o} \leq 0,02$$

$$\frac{12}{16} = \frac{D}{1-D} \quad \rightarrow 12 - 12D = 16D \quad \rightarrow D = \frac{3}{7}$$

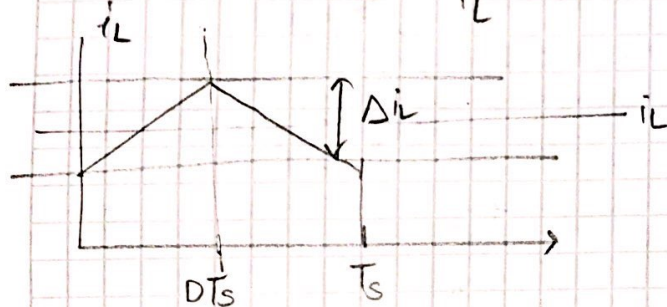a) L so that $\frac{\Delta i_L}{I_L} = 0,1$?



$$V_L = L \frac{di_L}{dt}$$

since the waveform is linear,


$$\frac{V_L}{L} = \frac{\Delta i_L}{\Delta t} \rightarrow \Delta i_L = \frac{V_L \Delta t}{L}$$

During the on cycle, the inductor will be charged.
Assuming that it charges up with i_{inave} will be misleading.
To find i_{Lave} , treat i_{in} as if it was nonzero for the entire period. $\rightarrow i_{Lave} = \frac{i_{inave}}{\frac{3}{7}} = \frac{\frac{3}{2}}{\frac{3}{7}} = 3,5$

we know $\Delta i_L = 3,5 \cdot 0,1 = 0,35 \text{ A}$

$$\Delta i_L = i_L(t_{on}) - i_L(0) = \frac{16 \text{ V} \cdot 3}{7 \cdot 50 \text{ kHz} \cdot L} = 0,35$$

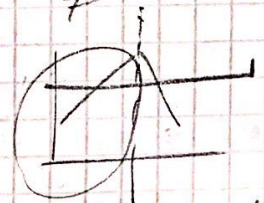
$$L = \frac{48}{0,35 \cdot 350 \text{ k}} \approx 0,392 \text{ mH}$$



our point of interest here, $i_{in} = i_L$. so, treat i_{in} to be nonzero across the entire period.

b) C so that $\frac{\Delta V_{out}}{V_{out}} = 0,02$?

Consider the ON cycle:

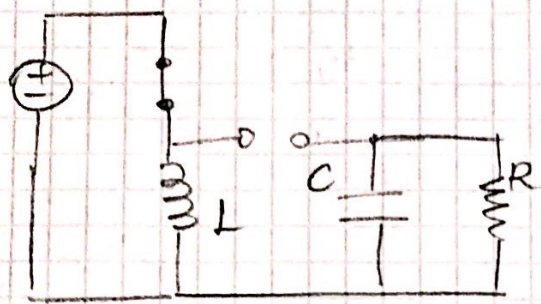

$$i_o = \frac{24W}{12V} = 2A$$

The capacitor will supply the output.
Assuming a constant current at the output

$$i_o = C \frac{\Delta V_o}{\Delta t}$$


$$2A = C \cdot \frac{\Delta V_o}{(DT_s)}$$

$$\frac{\Delta V_o}{V_o} = 0,02 \rightarrow \Delta V_o = 0,24$$

$$C = \frac{2 \cdot 3}{7,50k \cdot 0,24} \approx 71,43 \mu F$$

c) Choose commercial products.


ON

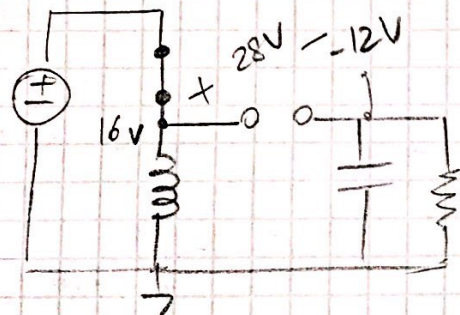

→ D should be able to withstand $-28V$.

→ The switch needs to allow an average current of $\frac{4}{3}A$.

OFF

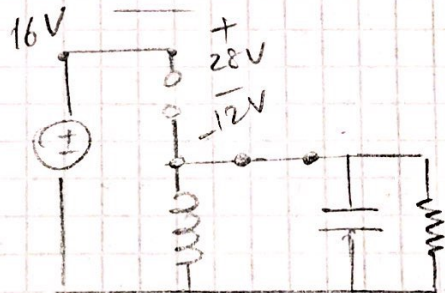


→ D should be able to carry $2A$ current.

→ The switch needs to be able to withstand $28V$.

- L → watch out for the current rating: $3,5A \pm 0,05\% \approx 3,675 A_{peak}$
- C → watch out for the voltage rating: $12V \pm 0,01\% = 12,12 V_{peak}$


Q2 | Cuk Converter

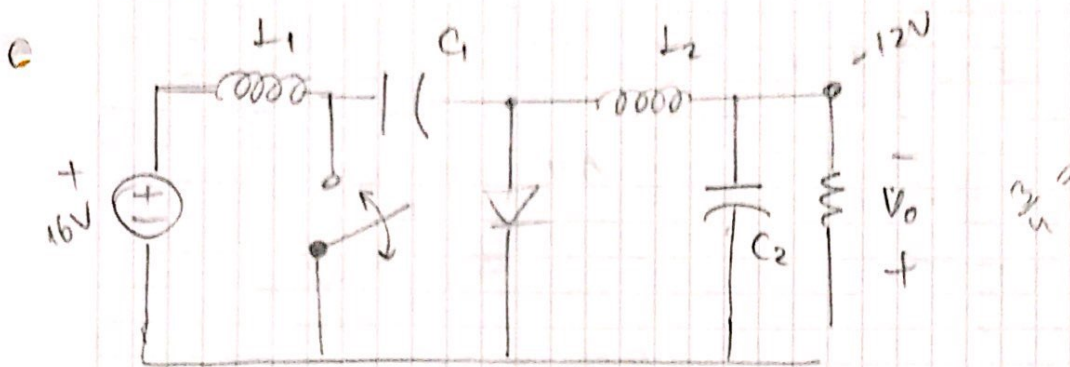

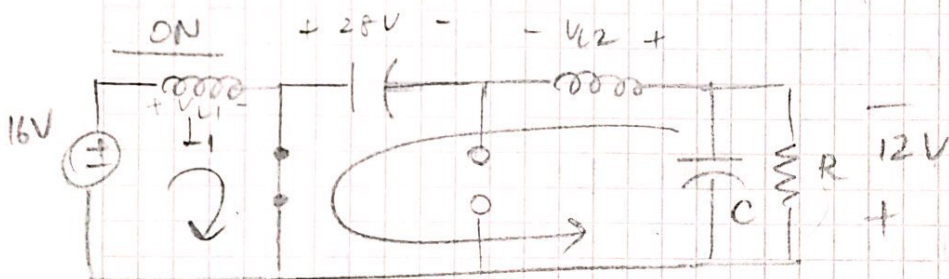a) Find C_2 by assuming 2% ripple and L_1 and L_2 by assuming 10% ripple.

once again, $\frac{V_0}{V_d} = \frac{D}{1-D}$, so the duty remains identical.

$$24W = 16 i_{in,ave} = 12 i_{out,ave} \quad \begin{cases} i_{in,ave} = \frac{3}{2} A \\ i_{out,ave} = 2A \end{cases}$$




L_2 this inductor will see a voltage of +16V.

$$\Delta i_{L2} = \frac{16V \cdot 3}{7.50kHz \cdot L_2}$$

$$\frac{\Delta i_{L2}}{i_{L2}} = \frac{48 \cdot 24}{350k \cdot L_2 \cdot 2} = \frac{1}{10}$$

$$L_2 = \frac{240}{350k}$$

$$L_2 \approx 0.686mH$$

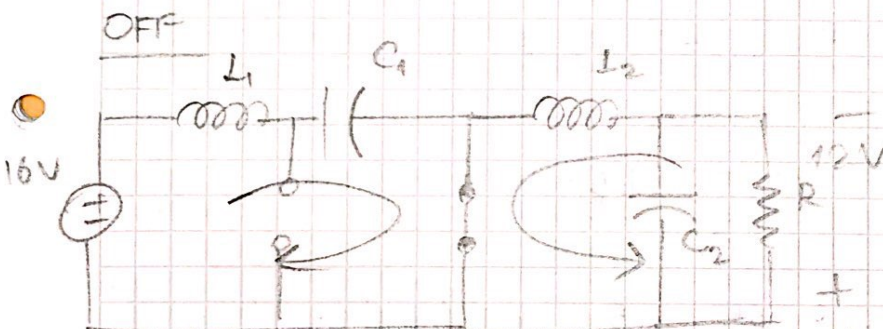

L_1 this inductor will see a voltage of +16V during the on cycle.

$$\Delta i_{L1} = \frac{16V \cdot 3}{7.50kHz \cdot L_1}$$

$$\frac{\Delta i_{L1}}{i_{L1}} = 0.1 \Rightarrow \frac{48V}{350k \cdot L_1 \cdot \frac{3}{2}} = \frac{1}{10}$$

$$\frac{320}{350k} = L_1$$


$$L_1 \approx 0.914mH$$

> verify in the discharge cycle:

$$\Delta i_{L1} = \frac{(16 - 28) \cdot 4}{7.50kHz \cdot L_1}$$

$$\approx 0.1509A \quad L_1 = 0.914mH$$

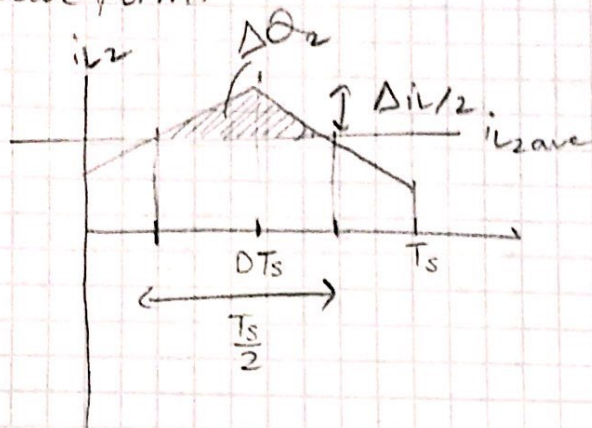We can find the V_{C2} ripple by considering the L_2 wave form.



$$\Delta Q_2 = \frac{\Delta i_{L2}}{2} \cdot \frac{T_s}{2} \cdot \frac{1}{2}$$

$$\Delta V_0 = \frac{\Delta Q_2}{C}$$

$$= \frac{\Delta i_{L2} T_s}{8 C_2}$$

$$\Delta V_0 = \frac{(1-D) T_s (-V_0) T_s}{8 L_2 C_2}$$

$$\frac{4 \cdot 1000}{7 \cdot (50k)^2 \cdot 8 \cdot 0,686 \cdot C_2} = 0,02 \quad \left| \frac{\Delta V_0}{V_0} \right| = \frac{(1-D) T_s^2}{8 L_2 C_2} = 0,02$$

$$\rightarrow C_2 \cong 2,082 \mu F$$

b) Find C_1 if $\frac{\Delta V_{C1}}{V_{C1}} = 0,1$

During the off cycle, L_1 discharges and C_1 charges.

> Assume it charges w/ a constant $I_{L1,ave}$.

$$\text{Then, } \frac{\Delta V_{C1}}{\Delta t} \cdot C_1 = i_{C1} = i_{L1,ave}$$


$$\Delta V_{C1} = \frac{(1-D) T_s \cdot I_{SA}}{C_1}$$

$$\frac{\Delta V_{C1}}{V_{C1}} = \frac{4}{7} \cdot \frac{1}{50k} \cdot \frac{3}{2} \cdot \frac{1}{C_1} \cdot \frac{1}{28} = \frac{1}{10}$$

$$\rightarrow C_1 = \frac{120}{350k \cdot 56}$$

$$\rightarrow C_1 = 12,45 \mu F$$

Q3 | SEPIC

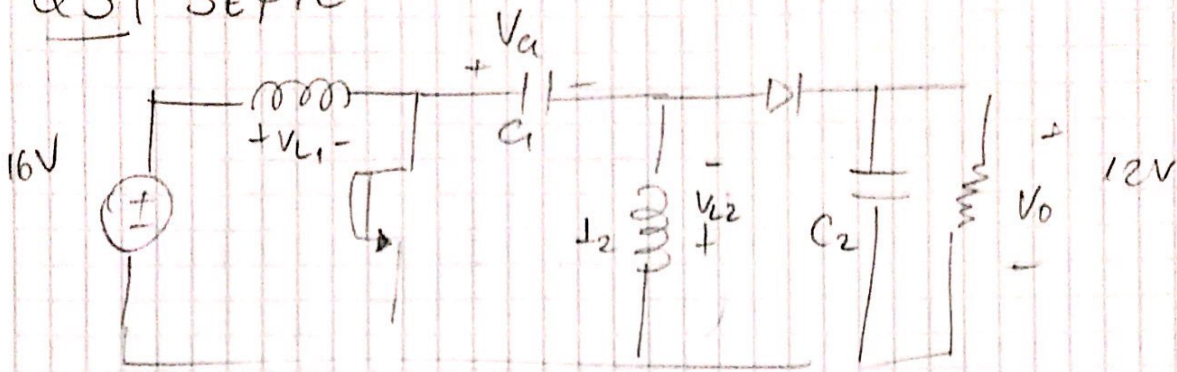

> same duty, once again. ($D = \frac{3}{7}$)
(same transfer function)

$$I_{Lave} = \frac{3}{2} A$$

a) L_1 and L_2 assuming 10% ripple?
 C_2 assuming 2% ripple?

ON cycle $\rightarrow L_1$ charges w/ $V_s = 16V$.

$$\Delta i_{L1} = \frac{16 \cdot 3}{7 \cdot L_1 \cdot 50k} = 0.15 \rightarrow L_1 = 0.914 mH$$

L_2 / In the off cycle, $i_D = i_{Lave} + i_{out}$. This implies i_{L2ave} must be i_{outave} .

In the on cycle, i_{L2} will increase w/ $V_{C1} = V_s = 16V$

$$\Delta i_{L2} = 0.2 = \frac{16 \cdot 3}{7 \cdot L_2 \cdot 50k} \rightarrow L_2 = 0.686 mH$$

C_2 / In the on cycle, C_2 will supply the output current. Assuming it to be constant at 2A.

$$\Delta V_o = \frac{2A \cdot 4}{7 \cdot C_2 \cdot 50k} = 0.24 \rightarrow C_2 = 95.238 \mu F$$

b) C_1 assuming $\Delta V_{C1} = 1.6$?

> in the on cycle, it will discharge to feed L_2 .
Assuming a constant current of 2A (i_{L2ave})

$$\Delta V_{C1} = \frac{2A \cdot 3}{7 \cdot 50k C_1} = 1.6 \rightarrow C_1 \approx 10.71 \mu F$$