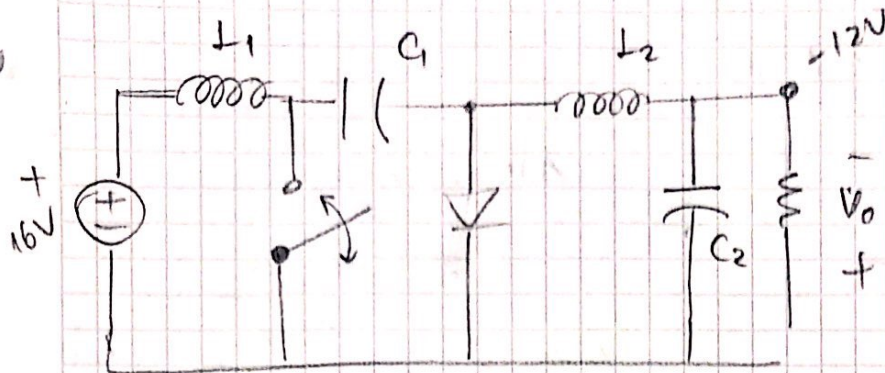



Q2/ Cuk Converter



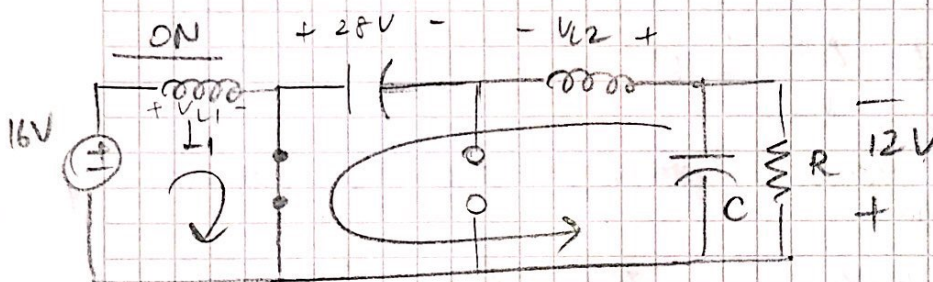a) Find C_2 by assuming 2% ripple and L_1 and L_2 by assuming 10% ripple.

once again, $\frac{V_o}{V_d} = \frac{D}{1-D}$, so the duty remains identical.

$$24W = 16 i_{in,ave} = 12 i_{out,ave} \quad \left\{ \begin{array}{l} i_{in,ave} = \frac{3}{2} A \\ i_{out,ave} = 2A \end{array} \right.$$




L_2 / this inductor will see a voltage of $\pm 16V$.

$$\Delta i_{L2} = \frac{16V \cdot 3}{7.50kHz \cdot L_2}$$

$$\frac{\Delta i_{L2}}{i_{L2}} = \frac{48 \cdot 24}{350k \cdot L_2 \cdot 2} = \frac{1}{10}$$

$$L_2 = \frac{240}{350k}$$

$$L_2 \approx 0.686mH$$

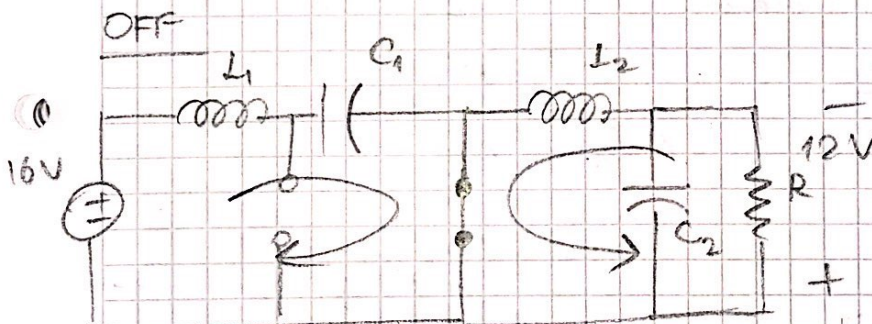

L_1 / this inductor will see a voltage of $\pm 16V$ during the on cycle.

$$\Delta i_{L1} = \frac{16V \cdot 3}{7.50kHz \cdot L_1}$$

$$\frac{\Delta i_{L1}}{i_{L1}} = 0.1 \Rightarrow \frac{48V}{350k \cdot L_1 \cdot \frac{3}{2}} = \frac{1}{10}$$

$$\frac{320}{350k} = L_1$$

$$L_1 \approx 0.914mH$$


> verify in the discharge cycle:

$$\Delta i_{L1} = \frac{(16 - 28) \cdot 4}{7.50kHz \cdot L_1}$$

$$\approx 0.1500V$$

$$L_1 = 0.914mH$$

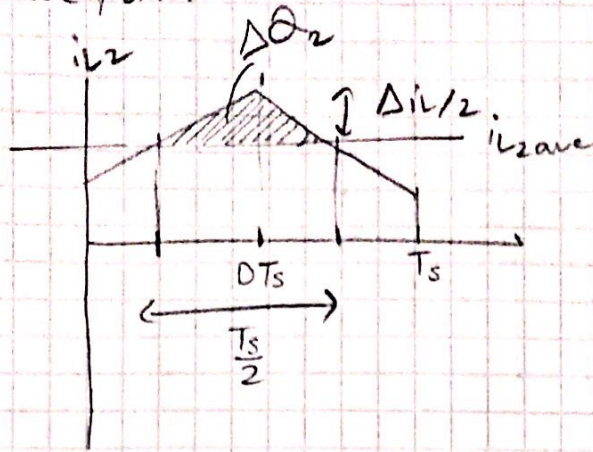We can find the V_{o2} ripple by considering the L_2 wave form.



$$\Delta Q_2 = \frac{\Delta i_{L2}}{2} \cdot \frac{T_s}{2} \cdot \frac{1}{2}$$

$$\Delta V_o = \frac{\Delta Q_2}{C} = \frac{\Delta i_{L2} T_s}{8 C_2}$$


$$\Delta V_o = \frac{(1-D) T_s (-V_o) T_s}{8 L_2 C_2}$$

$$\frac{4 \cdot 1000}{7 \cdot (50k)^2 \cdot 8 \cdot 0,686 \cdot C_2} = 0,02 = \left| \frac{\Delta V_o}{V_o} \right| = \frac{(1-D) T_s^2}{8 L_2 C_2} = 0,02$$

$$\rightarrow C_2 \approx 2,082 \mu F$$

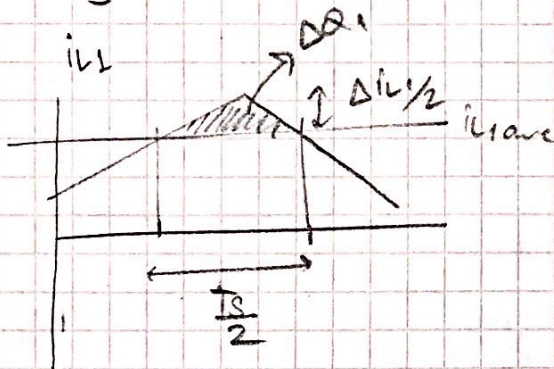b) Find C_1 if $\frac{\Delta V_{o1}}{V_{o1}} = 0,1$

During the off cycle, L_1 discharges and C_1 charges.



$$\Delta Q_1 = \frac{\Delta i_{L1}}{2} \cdot \frac{T_s}{2} \cdot \frac{1}{2}$$

$$= \frac{\Delta i_{L1} T_s}{8}$$

$$\Delta V_{o1} = \frac{\Delta Q_1}{C}$$

$$= \frac{(1-D) (-12) T_s \cdot T_s}{8 L_1 C_1}$$

$$0,1 = \left| \frac{\Delta V_{o1}}{V_{o1}} \right| = \frac{4 \cdot 12 \cdot 1000}{7 \cdot 8 \cdot 0,914 \cdot C_1 \cdot (50k)^2 \cdot 28}$$

$$\Rightarrow C_1 = \frac{480 \cdot 1000}{56 \cdot 0,914 \cdot (50k)^2 \cdot 28}$$

$$\approx 0,134 \mu F$$